

Chapter 32 Homework Problems


4. A solenoid of radius 2.50 cm has 400 turns and a length of 20.0 cm. Find (a) its inductance and (b) the rate at which current must change through it to produce an emf of $75.0 \mu\text{V}$.

9. The current in a 90.0-mH inductor changes with time as $I = 1.00t^2 - 6.00t$, where I is in amperes and t is in seconds. Find the magnitude of the induced emf at (a) $t = 1.00$ s and (b) $t = 4.00$ s. (c) At what time is the emf zero?


10. **M** An inductor in the form of a solenoid contains 420 turns and is 16.0 cm in length. A uniform rate of decrease of current through the inductor of 0.421 A/s induces an emf of $175 \mu\text{V}$. What is the radius of the solenoid?

15. A series RL circuit with $L = 3.00$ H and a series RC circuit with $C = 3.00 \mu\text{F}$ have equal time constants. If the two circuits contain the same resistance R , (a) what is the value of R ? (b) What is the time constant?

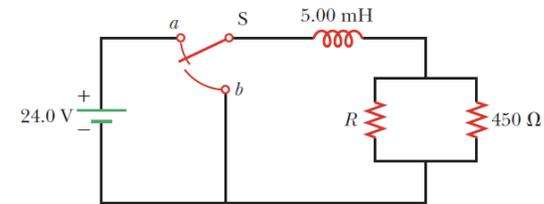
17. Consider the circuit shown in Figure P32.17. (a) When the switch is in position a , for what value of R will the circuit have a time constant of $15.0 \mu\text{s}$? (b) What is the current in the inductor at the instant the switch is thrown to position b ?



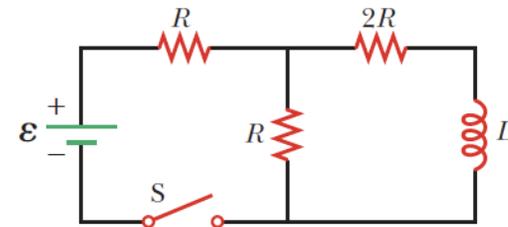21. The switch in Figure P32.21 is open for $t < 0$ and is then thrown closed at time $t = 0$. Assume $R = 4.00 \Omega$, $L = 1.00$ H, and $\mathcal{E} = 10.0$ V. Find (a) the current in the inductor and (b) the current in the switch as functions of time thereafter.



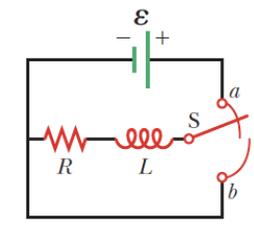
25. An inductor that has an inductance of 15.0 H and a resistance of $30.0\ \Omega$ is connected across a 100-V battery. What is the rate of increase of the current (a) at $t = 0$ and (b) at $t = 1.50\text{ s}$?



29. **M** An air-core solenoid with 68 turns is 8.00 cm long and has a diameter of 1.20 cm . When the solenoid carries a current of 0.770 A , how much energy is stored in its magnetic field?

30. A 10.0-V battery, a $5.00\text{-}\Omega$ resistor, and a 10.0-H inductor are connected in series. After the current in the circuit has reached its maximum value, calculate (a) the power being supplied by the battery, (b) the power being delivered to the resistor, (c) the power being delivered to the inductor, and (d) the energy stored in the magnetic field of the inductor.

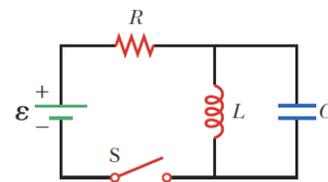43. In the circuit of Figure P32.43, the battery emf is 50.0 V , the resistance is $250\ \Omega$, and the capacitance is $0.500\ \mu\text{F}$. The switch S is closed for a long time interval, and zero potential difference is measured across the capacitor. After the switch is opened, the potential difference across the capacitor reaches a maximum value of 150 V . What is the value of the inductance?



44. Calculate the inductance of an LC circuit that oscillates at 120 Hz when the capacitance is $8.00\ \mu\text{F}$.
45. A $1.00\text{-}\mu\text{F}$ capacitor is charged by a 40.0-V power supply. The fully charged capacitor is then discharged through a 10.0-mH inductor. Find the maximum current in the resulting oscillations.